



Please write clearly in block capitals.

Centre number

Candidate number

Surname _____

Forename(s) _____

Candidate signature _____

I declare this is my own work.

A-level PHYSICS

Paper 3
Section B Electronics

Friday 5 June 2020

Afternoon

Time allowed: The total time for both sections of this paper is 2 hours. You are advised to spend approximately 50 minutes on this section.

Materials

For this paper you must have:

- a pencil and a ruler
- a scientific calculator
- a Data and Formulae Booklet.

Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- If you need extra space for your answer(s), use the lined pages at the end of this book. Write the question number against your answer(s).
- Do all rough work in this book. Cross through any work you do not want to be marked.
- Show all your working.

| For Examiner's Use | |
|--------------------|------|
| Question | Mark |
| 1 | |
| 2 | |
| 3 | |
| 4 | |
| 5 | |
| TOTAL | |

Information

- The marks for questions are shown in brackets.
- The maximum mark for this paper is 35.
- You are expected to use a scientific calculator where appropriate.
- A Data and Formulae Booklet is provided as a loose insert.



JUN2074083BE01

IB/M/Jun20/E8

7408/3BE

Section B

Answer all questions in this section.


0 1

Figure 1 shows part of a circuit that includes a 4-bit binary counter. The main inputs and outputs of the counter are shown.

The counter generates a sequence of binary codes representing the decimal numbers 0 to 7

Output Q_0 is the least significant bit of the binary codes.

Figure 1

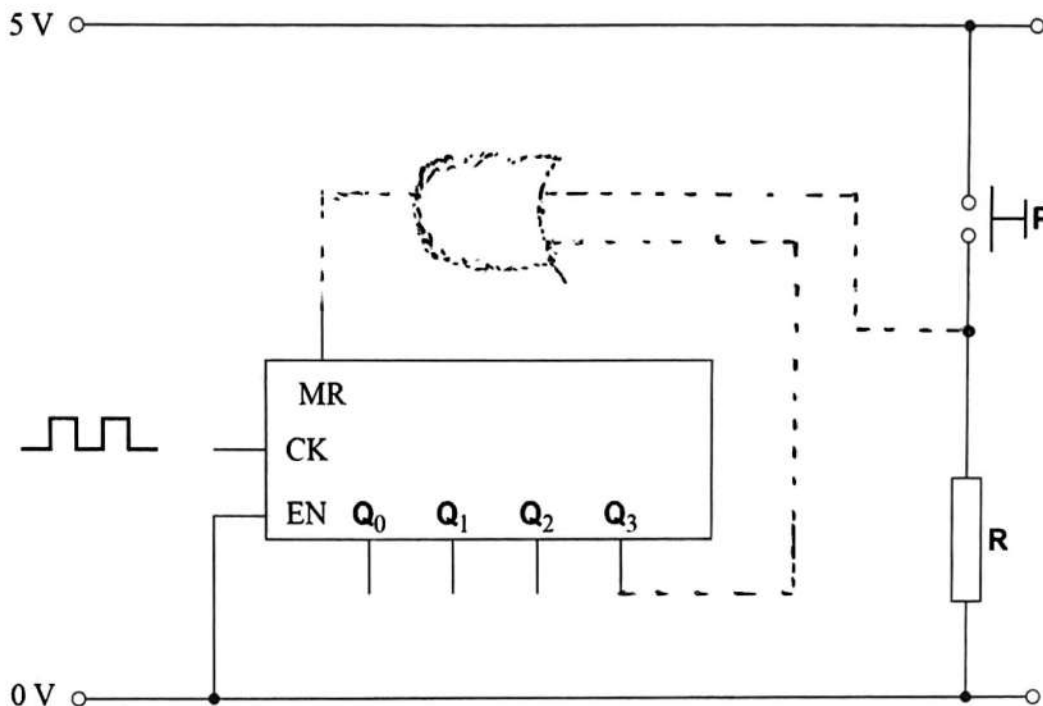

The counter resets when the master reset pin MR receives a logic 1

The circuit requires the counter to reset when either one of two conditions is met.

Condition 1 Manual reset using the switch P to reset the counter to 0

Condition 2 Automatic reset when an appropriate binary code is produced at the counter outputs. This will cause the counter to continually cycle through the decimal numbers 0 to 7

0 1 . 1

Complete **Figure 1** to show how both reset conditions can be met.

Do **not** show the power line connections to the integrated circuit.

[3 marks]

Question 1 continues on the next page

Turn over ►




0 1 . 2 A logic system is designed to identify prime numbers.

The binary codes from the counter are now applied to the inputs **ABC** of the logic system shown in **Figure 2**.

Input **A** takes the least significant bit of the binary code from the counter.

Output **W** becomes logic state 1 when a prime number 2, 3, 5 or 7 is detected. Otherwise output **W** is at logic 0

Figure 2

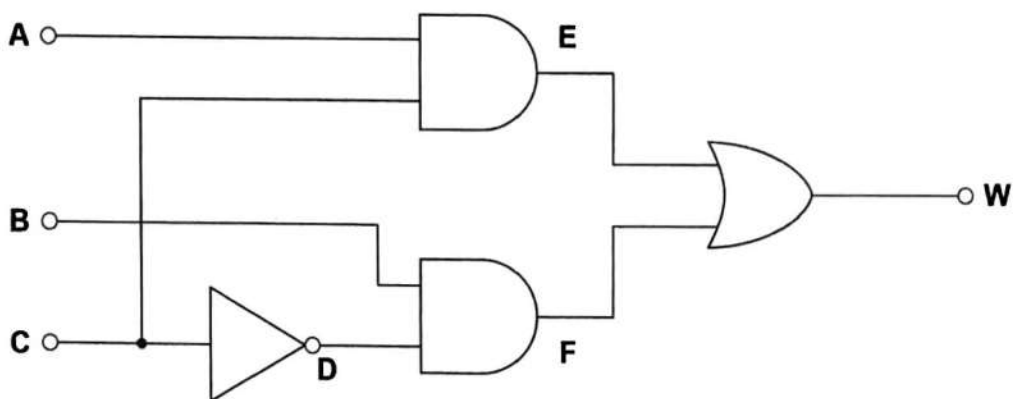

Write the Boolean algebra expression for output **W** in terms of the inputs **A**, **B** and **C**. The expression must contain only the four logic gate operations shown in **Figure 2**.

[2 marks]

$$w = (A \cdot C) + (B \cdot \bar{C})$$



Do not write
outside the
box

01.3 Complete Table 1, the truth table for the logic system in Figure 2.

[1 mark]

Table 1

| Decimal number | C | B | A | D | E | F | W |
|----------------|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 2 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 3 | 0 | 1 | 1 | 1 | 0 | 1 | 1 |
| 4 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 6 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 7 | 1 | 1 | 1 | 0 | 1 | 0 | 1 |

01.4 The logic system in Question 01.2 is replaced with one that gives an output **S** using the same binary input codes **CBA**.The Boolean algebra equation for output **S** is

$$S = \bar{A} \cdot (B + C)$$

Deduce which decimal numbers 0 to 7 will cause **S** to become logic 1

[1 mark]

numbers 2, 4 and 6

Question 1 continues on the next page

Turn over ►




Do not write
outside the
box

0 1 . 5 Complete **Figure 3** by drawing the logic system for **S**.

You must use only the logic gate operations given in $S = \bar{A} \cdot (B + C)$

[2 marks]

Figure 3

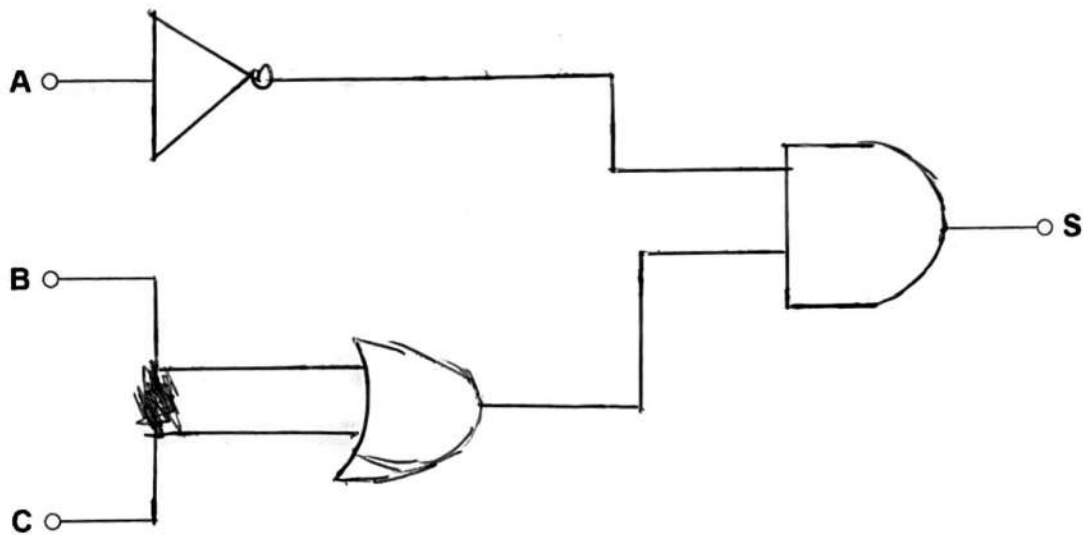

9




0 2

Figure 4 shows the filter circuit that forms the first stage in an amplitude modulated (AM) radio receiver.

The circuit contains a 3.3 mH inductor and a variable capacitor.

Figure 4

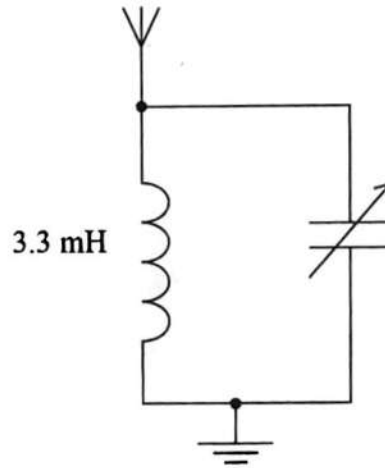

0 2 . 1

The circuit is tuned to receive a radio station transmitting at a frequency of 1053 kHz.

Calculate the value of the capacitance needed to receive this station.

[1 mark]

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$f^2 = \frac{1}{4\pi^2 LC}$$

$$C = \frac{1}{4\pi^2 f^2 L}$$

$$C = 6.92 \times 10^{-12}$$

capacitance = 6.9 pF



0 2 . 2

The circuit is retuned to receive a different radio station by setting the variable capacitor to a value of 9.3 pF.

Table 2 shows the capacitance range of four variable capacitors **W**, **X**, **Y** and **Z**.

Comment on the suitability of these capacitors for this application and state your preference.

[2 marks]

Table 2

| Capacitor | Range / pF |
|-----------|------------|
| W | 2–9 |
| X | 3–10 |
| Y | 4.5–20 |
| Z | 10–50 |

Y and X are most suitable as they're within the range. Y is better as it falls closer to the centre of the range.


Question 2 continues on the next page

Turn over ►



0 2 . 3 Figure 5 shows part of the frequency response curve for a different filter circuit.

Figure 5

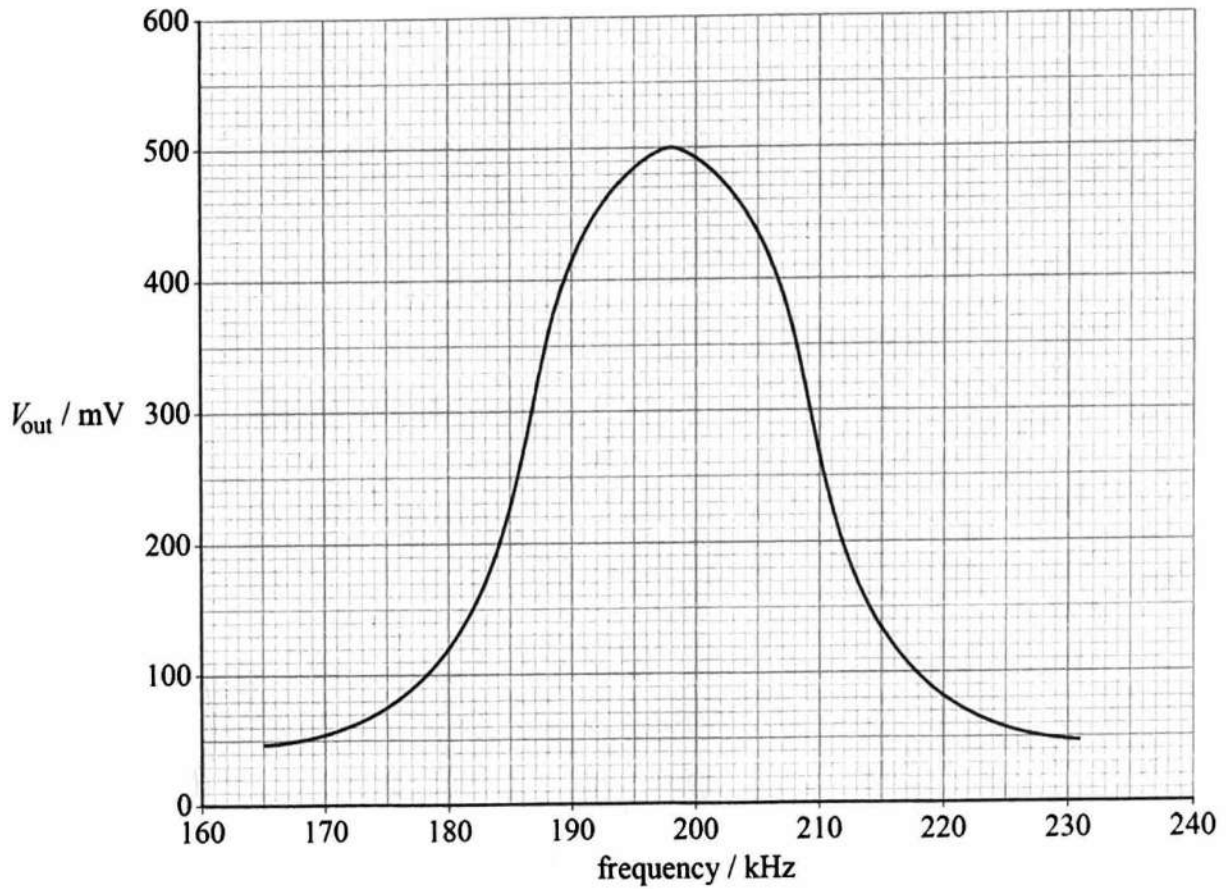

Determine the bandwidth of the filter circuit.

[2 marks]

$$0.7 \times V_{\max} = 0.7 \times 500 = 350$$

$$\text{At } 350, f = 187 \quad f = 207$$

$$207 - 187 = 20 \text{ kHz}$$

bandwidth = 20 kHz



Do not write
outside the
box

0 2 . 4 Calculate the Q factor of the filter circuit in Question 02.3.

[1 mark]

$$Q = f_0 / \Delta f = 198 \text{ kHz} / 20 \text{ kHz}$$

$$= 9.9$$

Q factor = 9.9

0 2 . 5 The radio station is tuned using a different filter circuit with a very low Q factor.

State and explain **one** effect of this change on the sound heard by a listener.

[1 mark]

Listeners will hear overlapping stations
due to the increase in bandwidth.

| |
|---|
| 7 |
|---|

Turn over for the next question

Turn over ►



0 3

Pulse code modulation (PCM) is used to encode live music as an uncompressed digital audio file.

Sampling of the analogue signal is carried out at 44.1 kHz.

A 16-bit system is used to encode each of the two channels that make up the stereo signal.

0 3 . 1

Explain why the sampling frequency used is suitable for this task.

[2 marks]

Range of frequencies for audio is 20 kHz,
and the sampling frequency should
be at least twice the max frequency.
It is 44.1 kHz, so is suitable.

0 3 . 2

Calculate the number of quantisation levels available on a 16-bit encoding system.

[1 mark]

$$2^{16} = 65536$$

number of quantisation levels = 65536



0 3 . 3 A recorded piece of stereo music lasts for 3.5 minutes.

Calculate the size, in megabytes, of the digital file needed to store this recording.

[2 marks]

$$f = 44.1 \text{ kHz}$$

$$44.1 \times 10^3 \times 16 \times (3.5 \times 60) = 1.48176 \times 10^8 \text{ mb}$$

$$= 148.176 \text{ mb}$$

For one channel

~~stereo~~ Stereo: $(2 \times 148) \div 8$

$$= 37.04$$

file size = 37.04 megabytes

0 3 . 4 The music file is used by a call centre to play as background music while a phone call is on hold. However, the telephone network is designed to use a bandwidth of 0.3 kHz – 3.4 kHz.

Compare the quality of the music heard by the telephone caller with that of the original file heard when played directly from a compact disc.

[2 marks]

There will be lower quality music over the telephone line because the telephone call has lower bandwidth than the original audio file. This means there is a loss of both low and high frequencies from the music.

7

Turn over ►




Do not write
outside the
box

0 4

Figure 6 shows a circuit containing a photodiode and an ideal operational amplifier. This circuit is used to monitor the intensity of monochromatic radiation.

Figure 6

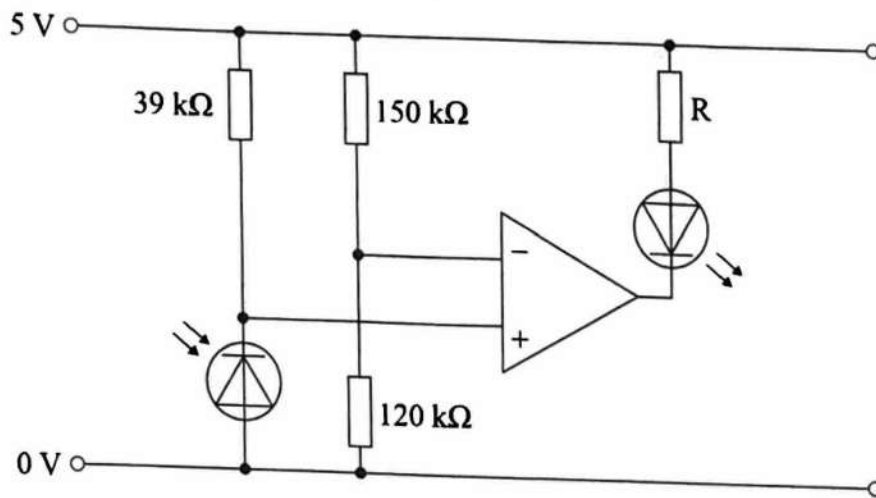

0 4 . 1

What is the configuration of the operational amplifier circuit shown in Figure 6? Tick (✓) one box.

[1 mark]

comparator

differential amplifier

inverting amplifier


non-inverting amplifier



04.2

Figure 7 shows the variation of photocurrent with intensity for the monochromatic radiation incident on the photodiode.

Figure 7

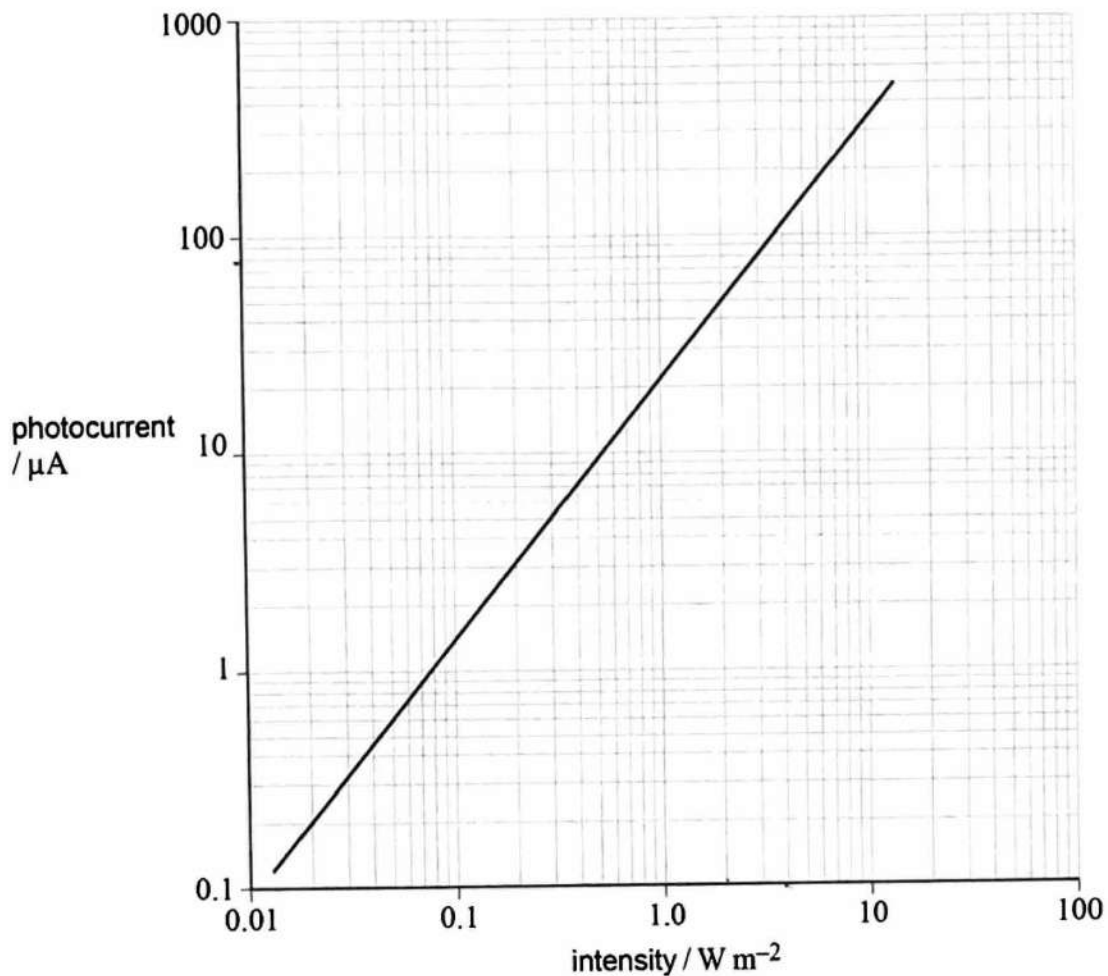

Radiation of intensity 3.0 W m^{-2} is incident on the photodiode.

Show that the voltage at the non-inverting terminal (V_+) of the operational amplifier is 1.9 V.

[3 marks]

At 3 W m^{-2} intensity, $80 \mu\text{A}$
is the photo current.

$$V_p = I \times R = 80 \times 10^{-6} \times 39 \times 10^3$$

$$V_R = 3.12 \text{ V} \quad \text{Voltage at non-inverting pin}$$

$$(V_+) = (5 - 3.12) = 1.88 \text{ V}$$

Question 4 continues on the next page

Turn over ►



0 4 . 3 The intensity of radiation incident on the photodiode remains at 3.0 W m^{-2} .

Deduce whether the light-emitting diode (LED) in Figure 6 is on or off.

[2 marks]

Voltage at inverting pin (V_-) = 2.2 V

$V_- > V_+$ because $2.2 > 1.9$.

So output is low, and LED is on.

6



0 5

British embassies in Europe are to be connected to a new long-distance communication link. The link, in the form of a land-based cable, will support multiple simultaneous video conferencing as well as the transmission of sensitive government data.

The company installing the link has to consider the choice between using optic fibre or copper wire in the cables.

Compare the advantages and disadvantages of the two options for use in these cables.

State which option you would advise the company to use.

For both types of cable refer to their:

- physical properties
- ability to reject external interference
- signal-carrying properties.

[6 marks]

Copper wire will corrode unless well protected, whereas glass doesn't corrode. Copper wire is also heavier than optic fibre, but optic fibre is more difficult to join sections. In terms of security, optic fibre cannot be tapped into unless broken, whereas optic copper cables can. Considering that the cables will be transmitting sensitive government data, optic fibres also can be used in noisy environments without noise interrupting signals which is again important ~~is~~ when transmitting important sensitive data. Copper wire is not immune to noise.

Question 5 continues on the next page

Turn over ►



The signal degradation is worse in copper wires. Also optic fibres have greater bandwidth and capacity. They are generally a lot better at carrying signals than copper cables.

With all this information, the clear choice is optic fibre cables. Due to the sensitive nature of the information and the simultaneous video conferencing, the cables will need to be reliable, with minimum interference and signal degradation. Optic fibre has the best properties.

END OF QUESTIONS

